

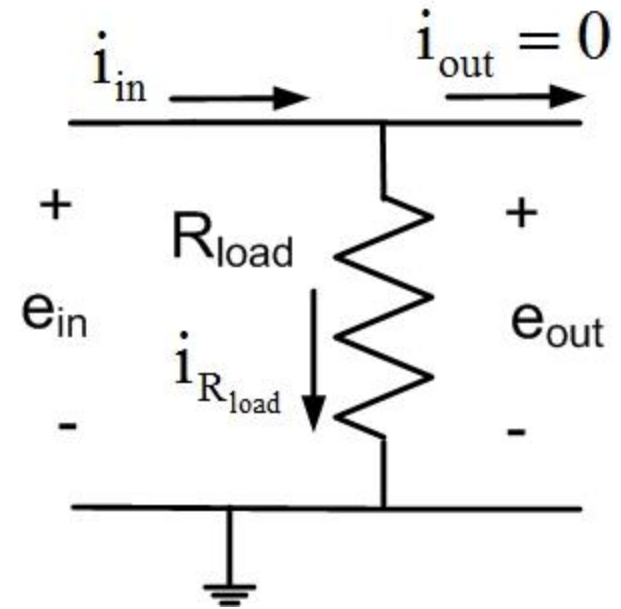


Loading of a Voltage Divider

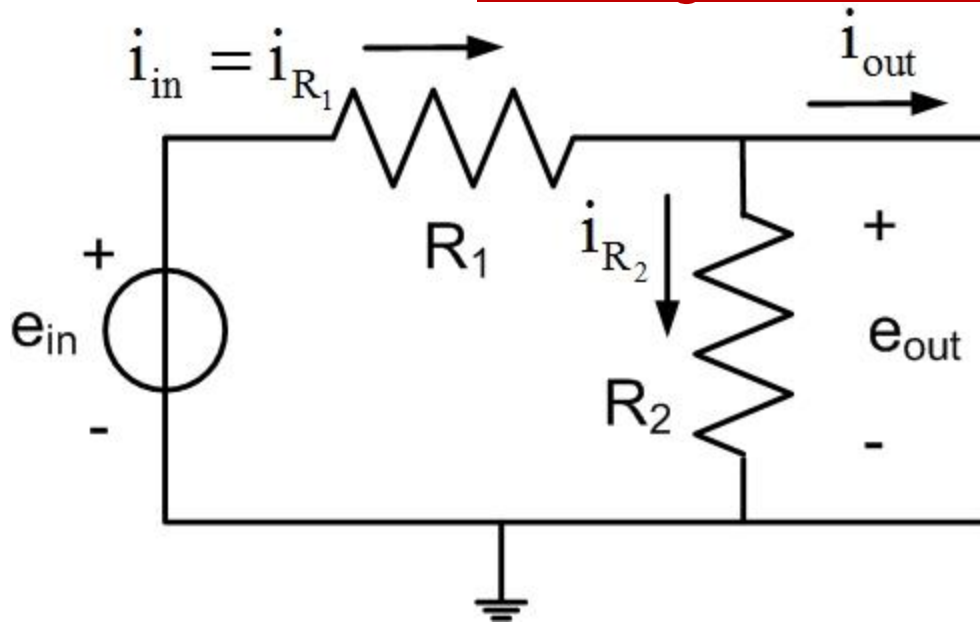

Voltage Divider with Buffer Op-Amp

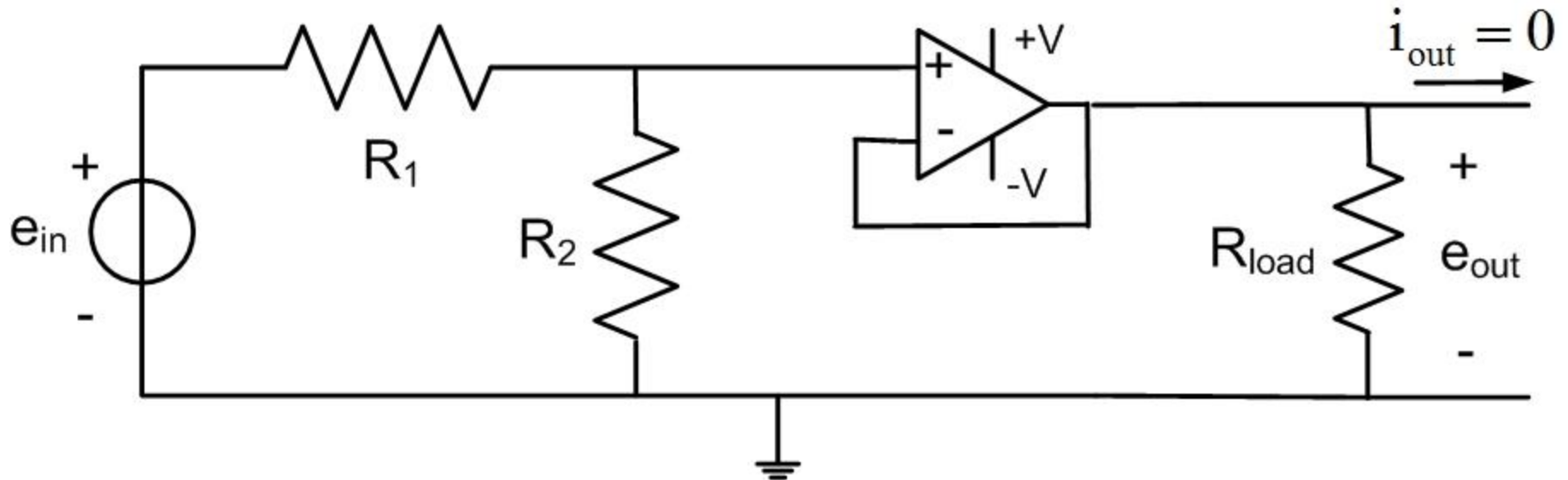

Loading of a Voltage Divider

$$e_{\text{out}} = e_{\text{in}} \frac{\frac{R_2 R_{\text{load}}}{R_2 + R_{\text{load}}}}{R_1 + \frac{R_{\text{load}} R_2}{R_2 + R_{\text{load}}}} = e_{\text{in}} \frac{\frac{R_2}{\frac{R_2}{R_{\text{load}}} + 1}}{R_1 + \frac{R_2}{\frac{R_2}{R_{\text{load}}} + 1}}$$

$$R_1 = R_2 = R_{\text{load}}$$

$$e_{\text{out}} = e_{\text{in}} \left(\frac{1}{3} \right)$$

Voltage Divider with Buffer Op-Amp

$$e_{\text{out}} = e_{\text{in}} \frac{R_2}{R_1 + R_2}$$


$$R_1 = R_2 = R_{\text{load}}$$

$$e_{\text{out}} = e_{\text{in}} \left(\frac{1}{2} \right)$$


Unity-Gain Buffer Op Amp

$e_{in} = e_{out}$ and in phase

Circuit Diagram
Representation

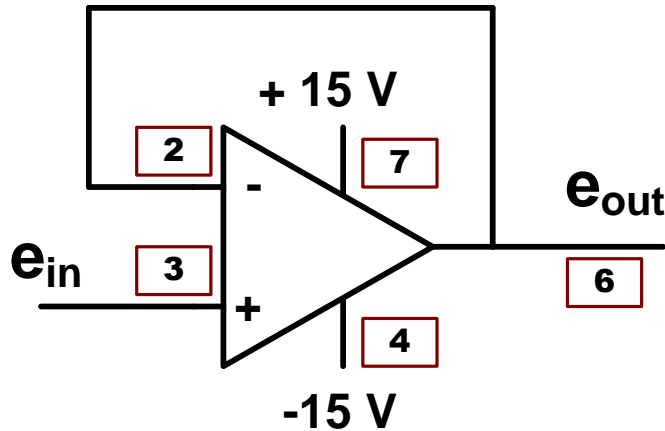

Wiring
Diagram

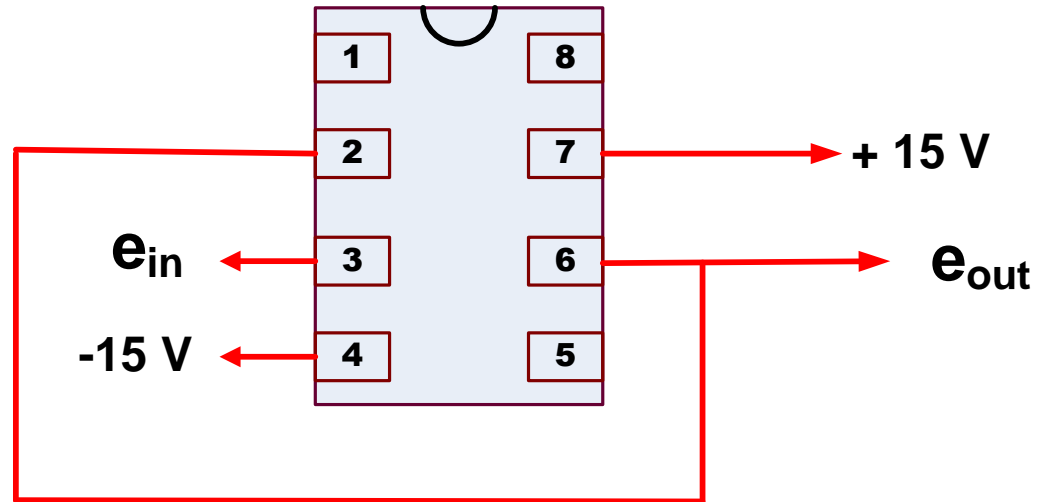

Input Impedance = ∞

Output Impedance = 0