

Name: _____ Session: _____

Draw the circuit diagram for the portion of the bread-boarded system shown below. Use the dual-op-amp, pin-out numbers 1 through 8 on your circuit diagram. (1 – output A, 2 – inverting input A, 3 – noninverting input A, 4 – -15V, 5 – noninverting input B, 6 – inverting input B, 7 – output B, 8 – +15V)

